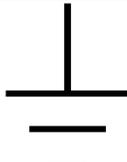
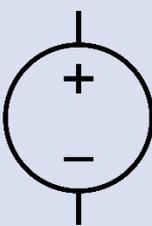


# Basic Electrical Engineering Information





## Introduction






Electrical engineering deals with electricity, electro-magnetism and electronics. It also covers power, control systems, telecommunications and signal processing. Electrical engineers are usually concerned with large-scale electrical systems such as motor control and power transmission, as well as utilizing electricity to transmit energy. Electrical engineers may work on a diverse range of technologies, from the design of household appliances, lighting and wiring of buildings, telecommunication systems, electrical power stations and satellite communications.

## Basic Elements of Circuit Analysis/Design

Term	Definition	Symbol/Unit
<b>Voltage</b>	The quantitative expression of the potential difference in charge between two points in an electrical field.	Volts or V
<b>Current</b>	The flow of electrons	Amperes or A
<b>Resistance</b>	The opposition that a substance offers to the flow of electric current	Ohms or $\Omega$
<b>Ground</b>	The reference point in the circuit where the voltage is 0.	
<b>Voltage Source</b>	A two terminal device which can maintain a fixed voltage	

# Components

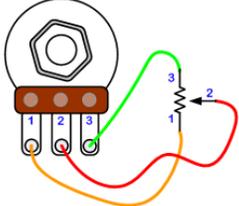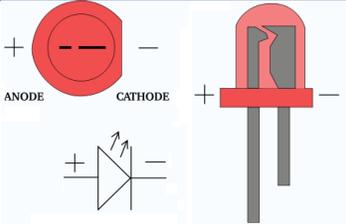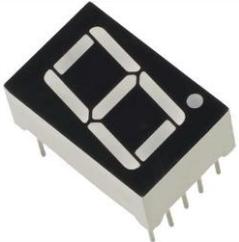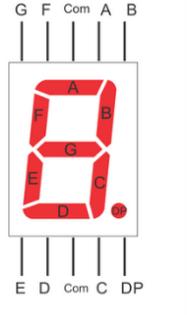Term	Definition	Picture	Layout
<b>Resistor</b>	A Component to control the current flow in a circuit.		
<b>Potentiometer</b>	A resistor which resistance value can be manually changed.		
<b>Photoresistor</b>	A resistor which resistance value is changed based on light. The resistance decreases with a higher light intensity		
<b>LED</b>	Light emitting diode, that is activated when a enough voltage is passed through it.		
<b>Seven Segment Display</b>	An electronic display device for displaying decimal numerals that is an alternative to the more complex dot matrix displays.		

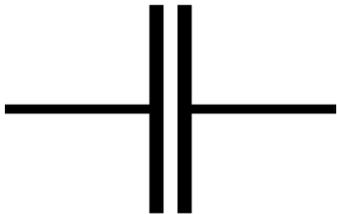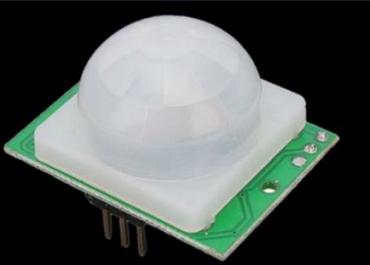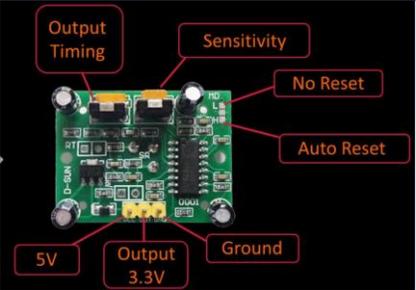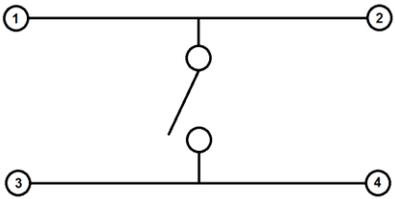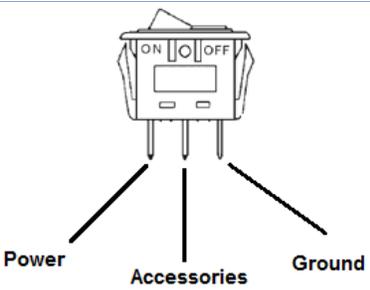	Com represents ground, and it must be connected to ground in order for the rest of the Lights to function		
<b>Capacitor</b>	A component that stores voltage in an electrical field		
<b>PIR Motion Sensor</b>	A Sensor that sends out a voltage if motion is detected		
<b>Tactile Button Switch</b>	A switch that can connect two components together through the press of the button.		
<b>Toggle Switch</b>	A switch that can connect two components together through the position of the switch		

# Fundamental Circuit Configurations

---

## Ohms Law

Ohm's Law deals with the relationship between voltage and current in an ideal conductor. This relationship states that:

The potential difference (voltage) across an ideal conductor is proportional to the current through it.

## Equation

$$V = IR$$

$$\text{Voltage} = \text{Current} * \text{Resistance}$$

## Series Circuits

Simple series circuits, all components are connected end-to-end to form only one path for electrons to flow through the circuit.

### Summary

- All components share the same current
- Resistance can be simplified by adding them together
  - $R_{\text{Total}} = R_1 + R_2 + \dots + R_n$

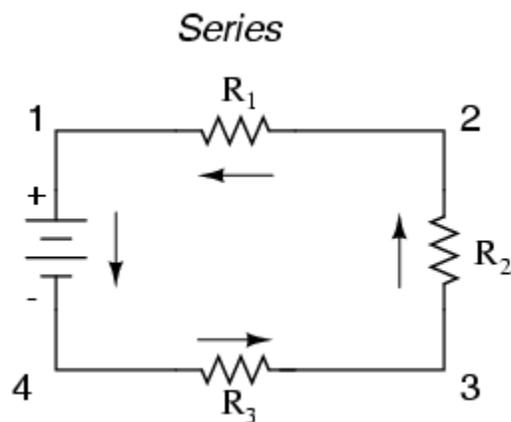


Figure 1 | Series Schematic

## Parallel Circuits

Simple parallel circuits, all components are connected between the same two sets of electrically common points, creating multiple paths for electrons to flow from one end of the battery to the other.

### Summary

- All components share the same voltage
- Resistance can be simplified by adding them together
  - $\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_1} + \dots + \frac{1}{R_n}$

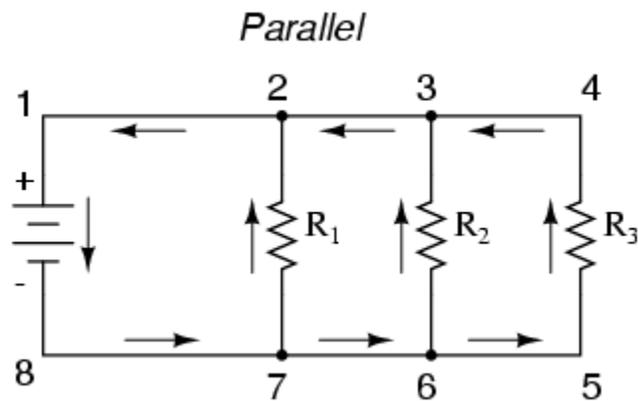


Figure 2 | Parallel Schematic

## Unit Table

TABLE 1.5 Selected Prefixes Used in the Metric System			
Prefix	Abbreviation	Meaning	Example
Giga	G	$10^9$	1 gigameter (Gm) = $1 \times 10^9$ m
Mega	M	$10^6$	1 megameter (Mm) = $1 \times 10^6$ m
Kilo	k	$10^3$	1 kilometer (km) = $1 \times 10^3$ m
Deci	d	$10^{-1}$	1 decimeter (dm) = 0.1 m
Centi	c	$10^{-2}$	1 centimeter (cm) = 0.01 m
Milli	m	$10^{-3}$	1 millimeter (mm) = 0.001 m
Micro	$\mu^a$	$10^{-6}$	1 micrometer ( $\mu\text{m}$ ) = $1 \times 10^{-6}$ m
Nano	n	$10^{-9}$	1 nanometer (nm) = $1 \times 10^{-9}$ m
Pico	p	$10^{-12}$	1 picometer (pm) = $1 \times 10^{-12}$ m
Femto	f	$10^{-15}$	1 femtometer (fm) = $1 \times 10^{-15}$ m

<sup>a</sup>This is the Greek letter mu (pronounced "mew").

Figure 3 | Metric System Table

## How to read a resistor

# Resistor Color Code

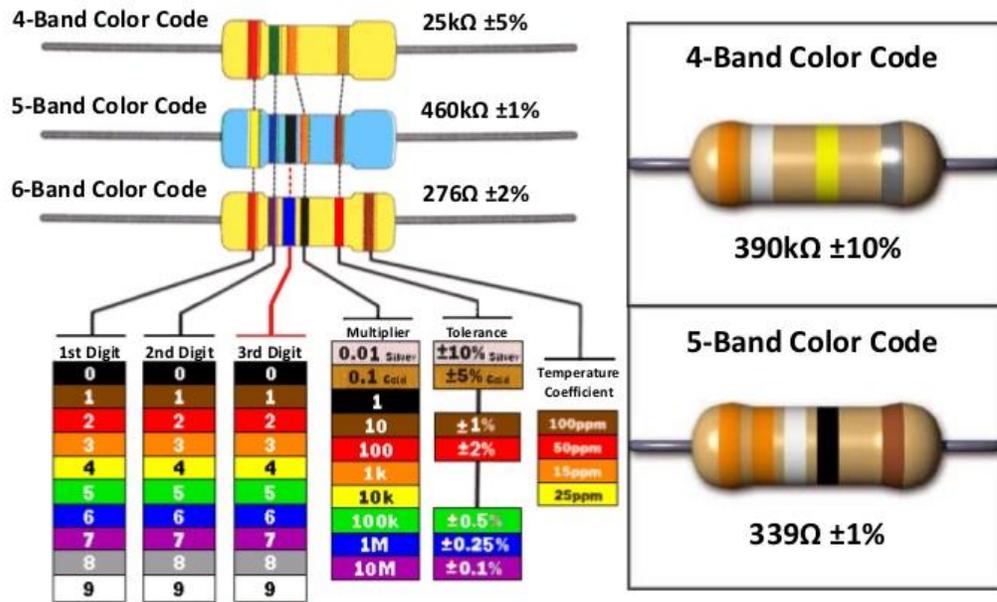


Figure 4 | Reading Resistor Guide

The 1<sup>st</sup> Color represents the 1<sup>st</sup> Digit represents the 100's place

The 2<sup>nd</sup> Color represents the 2<sup>nd</sup> Digit represents the 10's place

The 3<sup>rd</sup> Color represents the 3<sup>rd</sup> Digit represents the 1's place

The 4<sup>th</sup> Color represents the Multiplier

### Example

*To find a 420 MΩ*

1<sup>st</sup> Digit Color = Yellow = 400

2<sup>nd</sup> Digit Color = Red = 20

3<sup>rd</sup> Digit Color = Black = 0

4<sup>th</sup> Color = Blue = 1 Mega

$$(1^{\text{st}} \text{ Digit Color} + 2^{\text{nd}} \text{ Digit Color} + 3^{\text{rd}} \text{ Digit Color}) * 4^{\text{th}} \text{ Color} = (400 + 20 + 0) * 1\text{M} = 420\text{M}\Omega$$

# Digital Multimeter(DMM)

A digital multimeter (DMM) is a test tool used to measure two or more electrical values—principally voltage (volts), current (amps) and resistance (ohms). It is a standard diagnostic tool for technicians in the electrical/electronic industries.

## DMM Labels



Figure 5 | DMMs Settings

## How to Measure Voltage

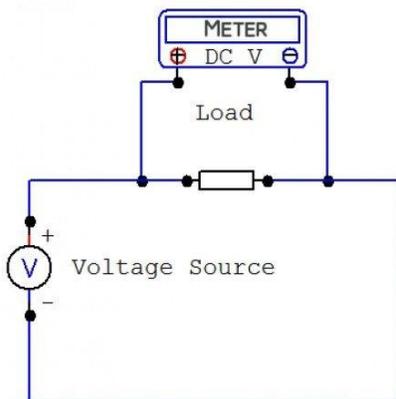


Figure 6 | Measuring Voltage

To measure voltage, the Digital Multimeter must be connected in **parallel** to the component that is being measured.

## How to Measure Current

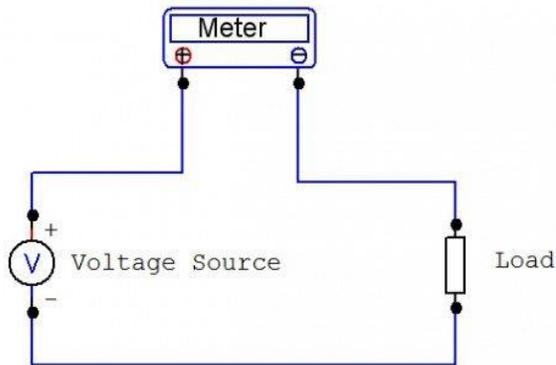



Figure 7 | Measuring Current

To measure current, the Digital Multimeter must be connected in **series** to the component that is being measured.

## Breadboard

A breadboard is a great tool for quickly testing out a prototype circuit or hooking up a quick experiment.

### How a Breadboard Works

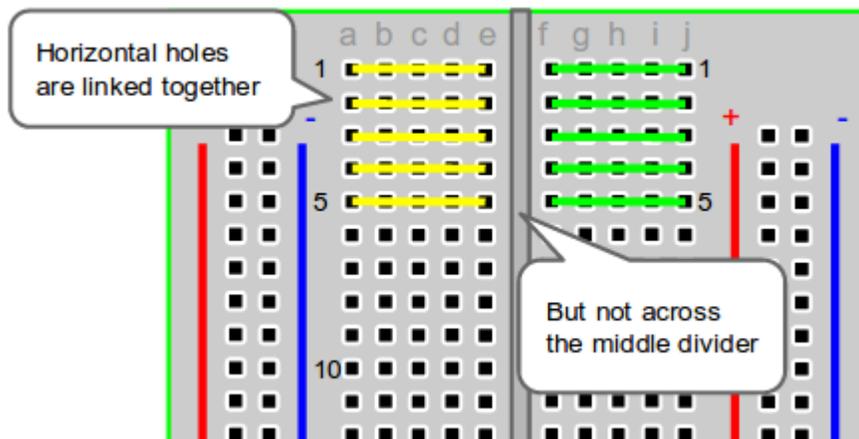

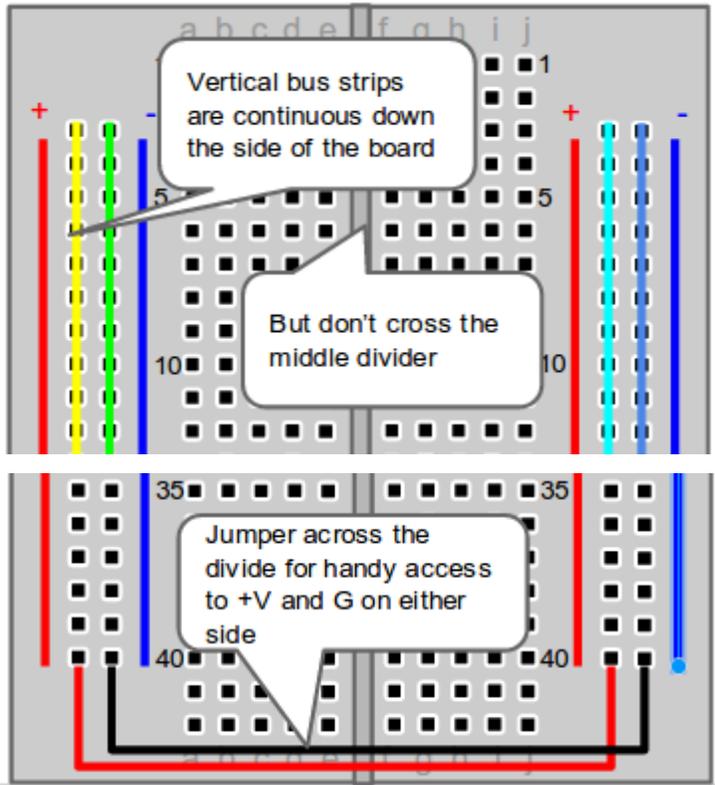


Figure 8 | How to use a Breadboard

Breadboard Example


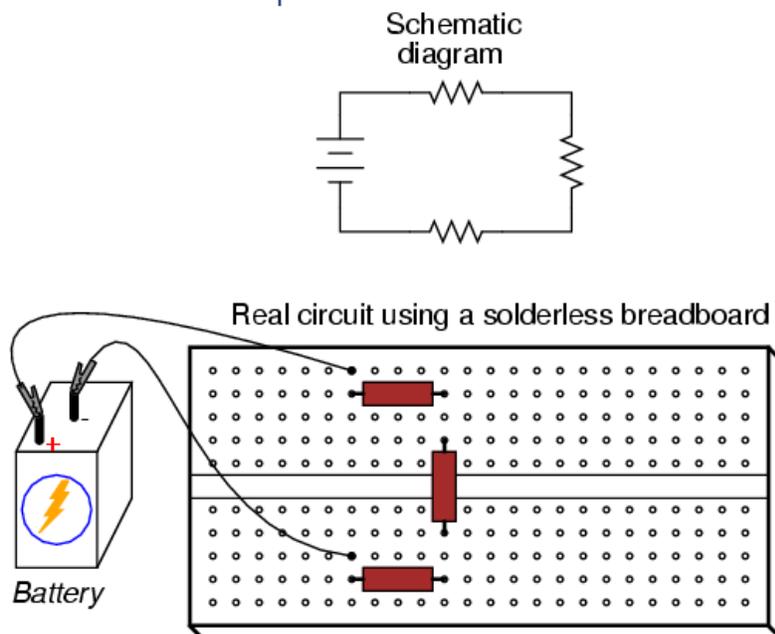


Figure 9 | A simple Series Circuit on a breadboard

Schematic diagram

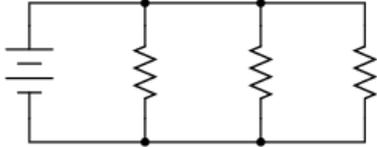

Real circuit using a solderless breadboard

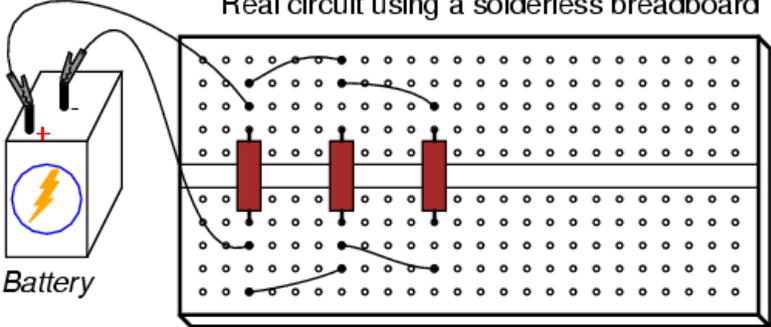


Figure 10 | A simple Parallel Circuit on a breadboard